



ECE2700J Introduction to Logic Design

Homework 3

Assigned: October 21, 2024



Due: October 28, 2024, 4:00pm

Submit a hard copy before the lecture begins.


*Note: you may ignore the propagation delays when drawing a timing diagram unless required differently.*

- (15 points) Design a 4-bit register with an external signal “R\_L”, such that when  $R\_L = 1$ , content of the 4-bit register is rotated to the left by 1 bit upon a clock edge (e.g. 1011 becomes 0111), and when  $R\_L = 0$ , the register works as normal. Use building blocks.

 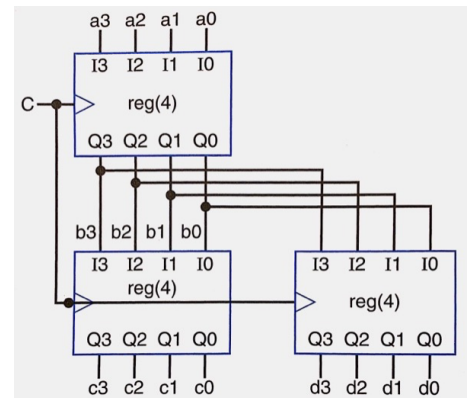- (15 points) Consider three 4-bit registers connected as in the figure on right. Assume the initial values in the registers are unknown. Trace the behavior of the registers by completing the following timing diagram.




 - (20 points) Describe in Verilog an 8-bit 4-to-1 MUX implemented with 2-to-1 MUXes. Simulate your design with a testbench.




**NOTE: the following problems are optional and won't be graded.**

 4. Model the circuit described in Problem 1 with Verilog HDL. Write a testbench to simulate your design.
5. Fill in the timing diagram below for a falling-edge triggered J-K flip-flop. Assume Q begins at 0.



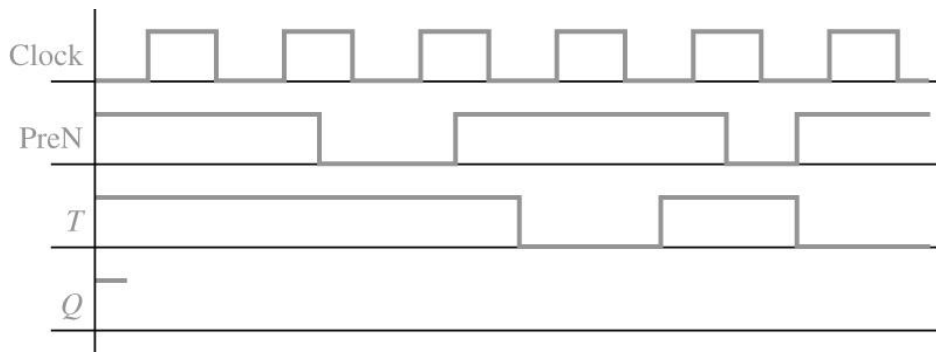6. Fill in the following timing diagram for a rising-edge triggered T flip-flop with an asynchronous active-low preset input (PreN, equivalent to set). Assume Q begins at 1.



7. Model the T flip-flop described in above problem in Verilog HDL. Then write a testbench to simulate your designed module and generate the exactly same timing diagram.